

PRACTICAL 4A: SEQUENTIAL CIRCUITS

Ronak Mehta (MHTRON001)

Plagiarism Declaration

1. I know that plagiarism is wrong. Plagiarism is to use another's work and pretend that it is one's own.
2. I have used the IEEE convention for citation and referencing. Each contribution to, and quotation in, this practical report from the work(s) of other people has been attributed and has been cited and referenced.
3. This practical report (including circuit diagrams and code) is my own work.
4. I have not allowed, and will not allow, anyone to copy my work with the intention of passing it off as their own work.
5. I acknowledge that copying someone else's code, schematics or report, or part of it, is wrong, and declare that this is my own work.



Signature

15-05-2018

Date

Solutions

PART 1:

(a)

The system has 4 states namely 2, 4, 6 and 8.


Number of bits == $(\log_2 4 = 2)$ == Number of D-Flip Flops in the system

States	State Number
2	00
4	01
6	10
8	11

Present State/Next State Diagram

INPUT	PRESENT STATE		NEXT STATE	
	Q_1	Q_0	D_1	D_0
0	0	0	0	1
0	0	1	1	0
0	1	0	1	1
0	1	1	0	0
1	0	0	1	1
1	0	1	1	0
1	1	0	0	0
1	1	1	0	1

(b) Equations from Karnaugh Maps

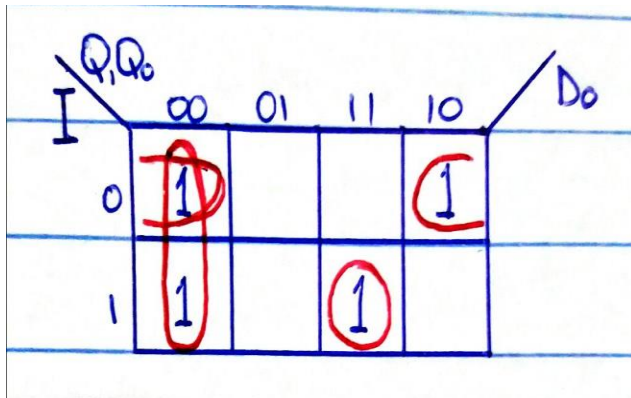

$$D_0 = (\overline{Q_1} \cdot \overline{Q_0}) + (\overline{I} \cdot \overline{Q_0}) + (I \cdot Q_1 \cdot Q_0)$$

$Q_1 Q_0$		D_1			
I		00	01	11	10
	0		1		1
	1	1	1		

$$D_1 = (\overline{Q_1} \cdot Q_0) + (I \cdot \overline{Q_1}) + (\overline{I} \cdot Q_1 \cdot \overline{Q_0})$$

Table for Output Logic expression

PRESENT STATE		OUTPUTS			
Q_1	Q_0	O_3	O_2	O_1	O_0
0	0	0	0	1	0
0	1	0	1	0	0
1	0	0	1	1	0
1	1	1	0	0	0

Expressions for the Output


$$O_3 = Q_1 \cdot Q_0$$

$$O_2 = Q_1 \oplus Q_0$$


$$O_1 = \overline{Q_0}$$

$$O_0 = 0$$

(c)

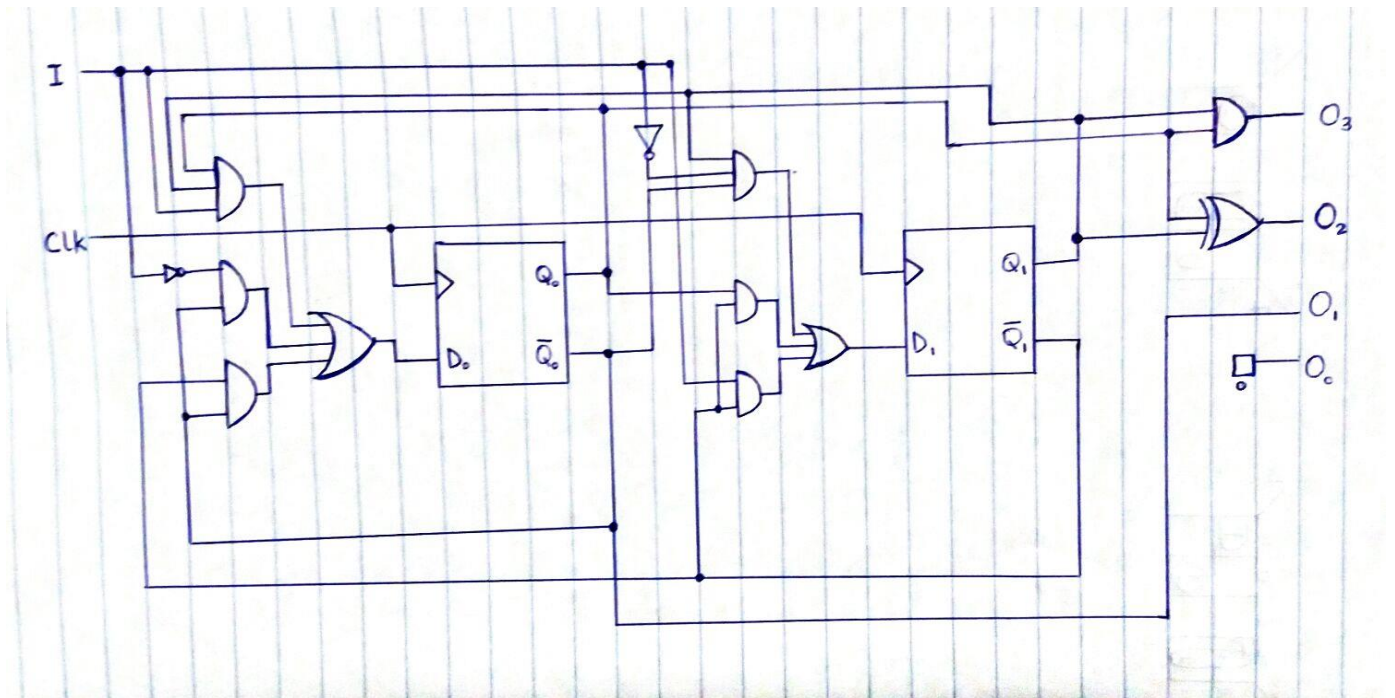


d) Screenshot of Circuit diagram from Logisim

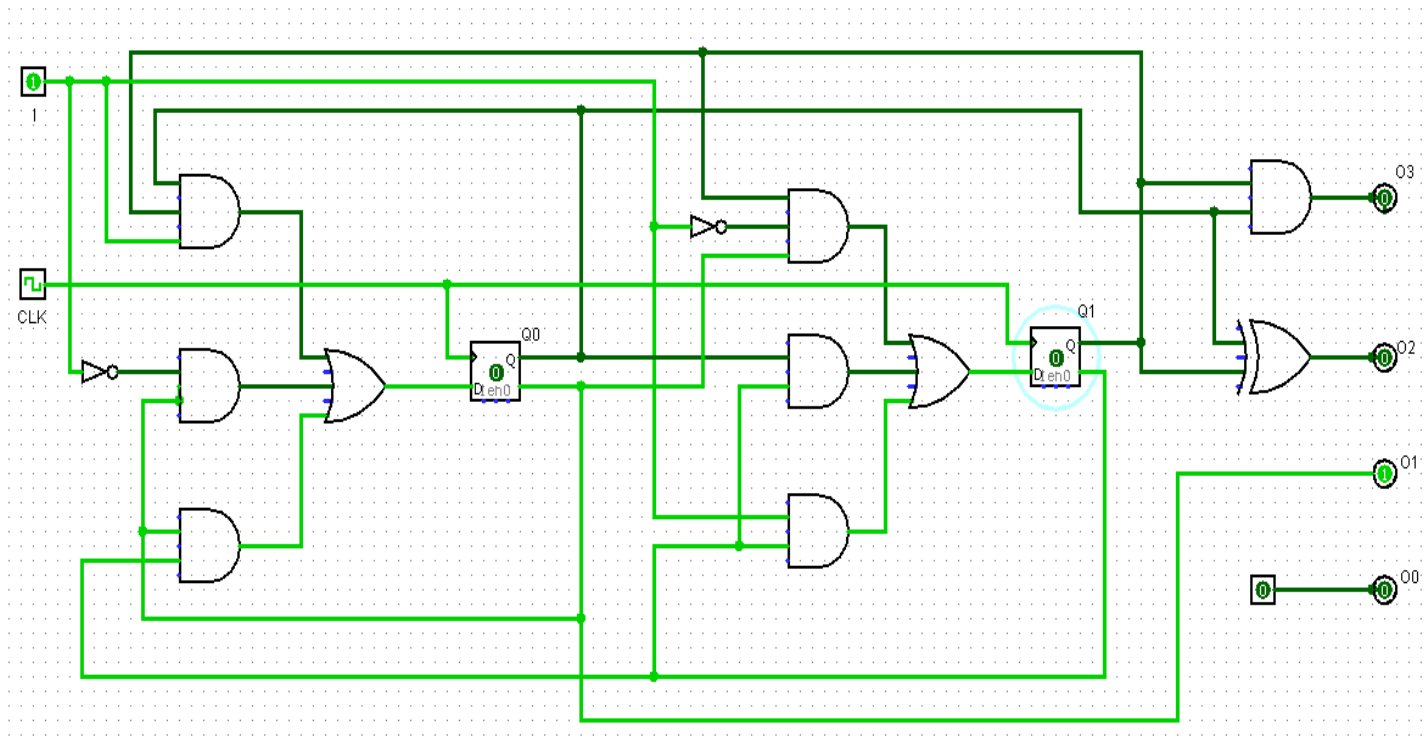


PART 2:

(a)

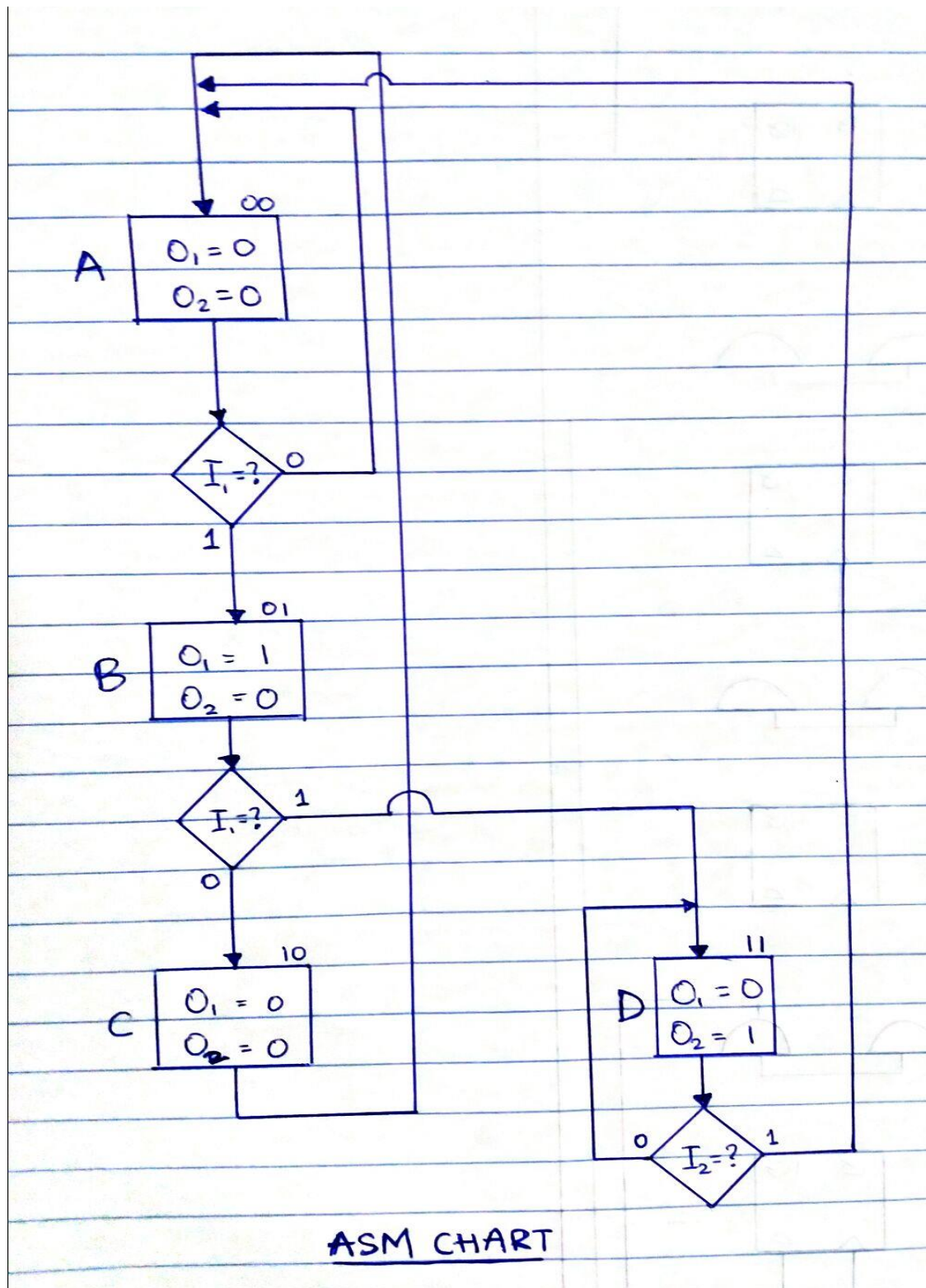

(b)

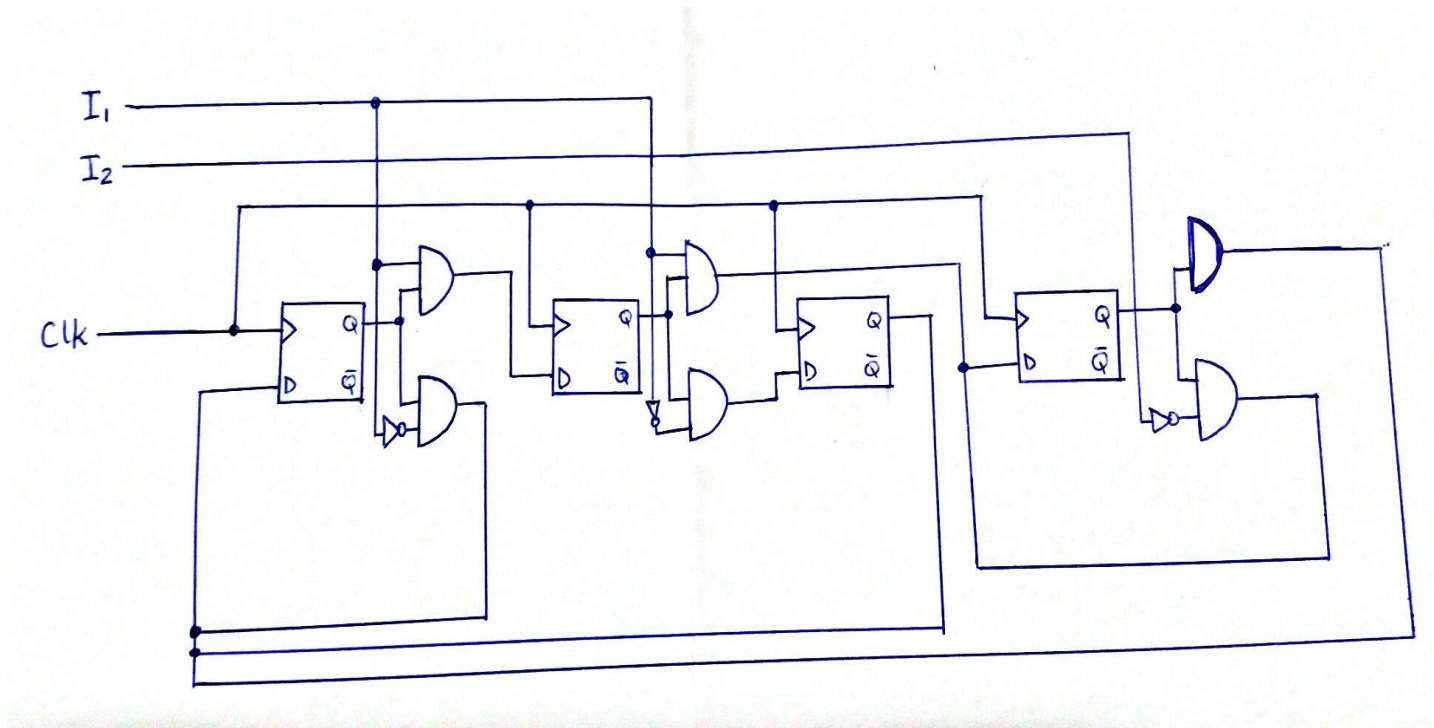

(c) Screenshot of circuit diagram from Logisim

