

# EEE4117F: ONLINE QUIZ 1

---

## ELECTRICAL MACHINES AND POWER ELECTRONICS



Prepared By:

**Ronak Mehta - MHTRON001**

Faculty of Engineering and the Built Environment

**09<sup>th</sup> May 2020**

## PART A – ELECTRICAL MACHINES

Question 1:

PART A:

Question 1:

- a) Match between motor and Load
- b) Thermal consideration in motor selection
- c) Control and current limiting.

⇒ Motor current ripple can be reduced by either adding a capacitor or providing ramp limiters which helps to prevent drives from tripping under sudden changes.



## Question 2:

Question 2:

$$\omega_m = 1000 \text{ rpm} \Rightarrow 1000 \times \frac{2\pi}{60} = \underline{104.72 \text{ rad/s}}$$

$$T = 40 \text{ secs}$$
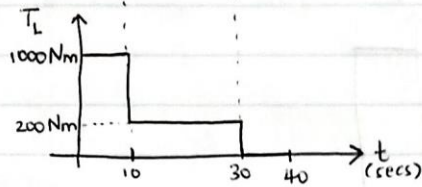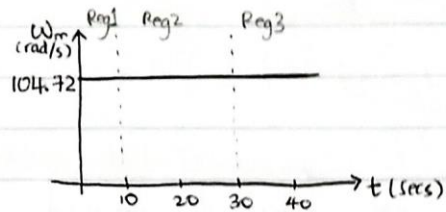
$$\dot{\omega}_m = 0 \text{ (constant speed)}$$




$$Q2 (1.1) \quad T_m = J \dot{\omega}_m + B \omega_m + T_L$$

Ignoring Damping effects:

$$T_{m1} = 0 + 0 + T_{L1} = T_{L1} = \underline{1000 \text{ Nm}}$$

$$T_{m2} = 0 + 0 + T_{L2} = T_{L2} = \underline{200 \text{ Nm}}$$
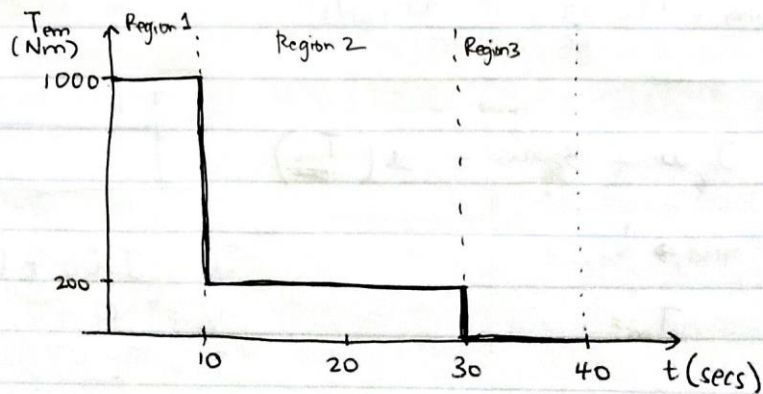
$$T_{m3} = 0 + 0 + T_{L3} = T_{L3} = \underline{0 \text{ Nm}}$$



Torque profile of motor-Load System

$$Q2(1.2) \quad T_{rms} = \frac{1}{T_{period}} \int_0^{T_{period}} T_{em}^2(t) \cdot dt$$

$$T_{rms} = \sqrt{\frac{(T_{em1}^2 \cdot t_1) + (T_{em2}^2 \cdot t_2) + (T_{em3}^2 \cdot t_3)}{t_1 + t_2 + t_3}}$$

$$T_{rms} = \sqrt{\frac{1000^2(10) + (200)^2 20 + 0^2(10)}{10+20+10}}$$

$$T_{rms} = 519.6 \text{ Nm}$$

$$P = T_{rms} \cdot \omega_m$$

$$P = 519.6 (104.72) = 54.4 \text{ kW}$$

$$P = 54.4 \text{ kW}$$

$$Q2(1.3) \quad P_{rot} \approx 0.1(54.4 \text{ kW}) = 5.44 \text{ kW}$$

$$k = 4 \text{ Nm/A} ; R_m = 0.267 \Omega / \text{phase} \Rightarrow \text{For 3 phase: } R_m = 3(0.267) \Omega$$

$$I_{rms} = \frac{T_{rms}}{k} = \frac{519.6 \text{ Nm}}{4 \text{ Nm/A}} = 129.9 \text{ A}$$

$$P_{cu} = I_{rms}^2 \cdot R_m$$

$$P_{cu} = (129.9)^2 \cdot 3(0.267) = 13.52 \text{ kW}$$

$$P_{cu} = 13.52 \text{ kW}$$

$$P_{loss} = P_{rot} + P_{cu} = 5.44 \text{ kW} + 13.52 \text{ kW} = 18.96 \text{ kW}$$

$$P_{loss} = 18.96 \text{ kW}$$

**PART B – POWER ELECTRONICS**

Question 1:



PART B:Question 1

$$V_{CE(sat)} = 0.2V$$

$$V_{BE(sat)} = 0.7V$$

$$\beta = 25-40$$

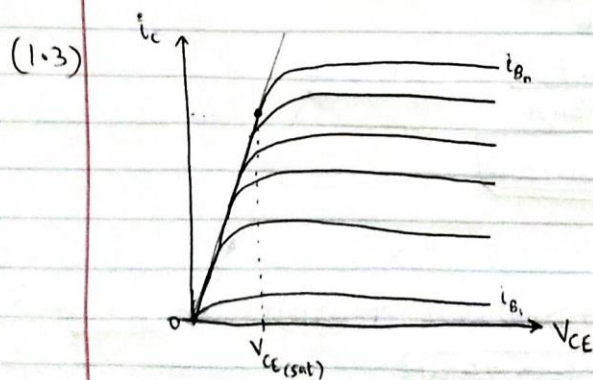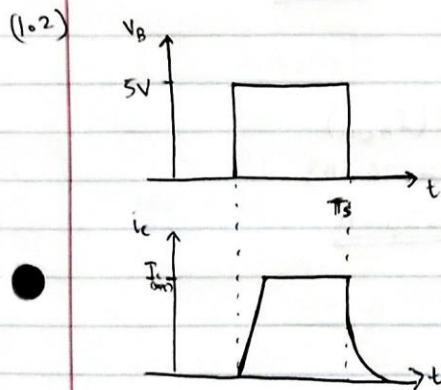- (1.1) The diode, D allows the current to only pass through one direction and thus <sup>in opposite direction</sup> blocking current, if leakage current is available which might be harmful for the transistor and can also lead to breakage of the transistor.





(1.4) From KVL:

$$V_{CC} = I_{C(sat)} R_C + V_{CE(sat)}$$

$$I_{C(sat)} = \frac{V_{CC} - V_{CE(sat)}}{R_C}$$

$$I_{C(sat)} = \frac{(24 - 0.2)V}{200\Omega} = \cancel{0.119} 0.119 A$$

$$\boxed{I_{C(sat)} = 0.119 A}$$

(1.5) ODF = 3

$$I_{B(sat)} = \frac{I_{C(sat)}}{\beta} = \frac{0.119}{25} = \underline{4.76 mA}$$

$$\begin{aligned} ODF &= \frac{I_B}{I_{B(sat)}} \Rightarrow I_B = ODF(I_{B(sat)}) \\ &= 3(4.76 mA) \\ \underline{I_B} &= \underline{14.28 mA} \end{aligned}$$

From KVL:

$$V_B = I_B R_B + V_{BE(sat)}$$

$$R_B = \frac{V_B - V_{BE}}{I_B} = \cancel{301.12 \Omega}$$

$$R_B = \frac{(5 - 0.7)V}{14.28 mA} = \underline{301.12 \Omega}$$

$$\therefore \boxed{R_B = 301.12 \Omega}$$

(1.6)  $P_{total} = P_{R_B} + P_{R_C}$ 

$$= I_B^2 R_B + I_{C(sat)}^2 R_C = (14.28 mA)^2 301.12 + (0.119)^2 200 = \underline{2.89 W}$$

$$\boxed{P_{Tot} = 2.89 W}$$

Question 2:

PART B:Question 2

$$(2.1) \quad \text{THD} = \sqrt{\left(\frac{I_{2h}}{I_{21}}\right)^2} * 100\%$$

$$= \sqrt{\left(\frac{1}{3}\right)^2 + \left(\frac{1}{5}\right)^2 + \left(\frac{1}{7}\right)^2 + \left(\frac{1}{9}\right)^2 + \left(\frac{1}{11}\right)^2 + \left(\frac{1}{13}\right)^2} * 100\%$$

$$\boxed{\text{THD} = 44.5\%}$$

$$(2.2) \quad \text{PF} = \frac{1}{\sqrt{1 + \text{THD}^2}}, \text{ DPF}$$

$$\text{PF} = \frac{1}{\sqrt{1 + 0.445^2}} * 1 = \cancel{0.825} 0.914$$

$$\boxed{\text{PF} = 0.914}$$