

# Practical 5: ALU

Ronak Mehta (MHTRON001) and Vikyle Naidoo (NDXVIK005)  
University of Cape Town, South Africa  
EEE3096S – 2019

**Abstract** - This practical was aimed at understanding the Arithmetic Logical Unit (ALU) and the variety of arithmetic, logical and bit shift operations it can perform.

## I. ALU DESIGN

 


Figure 1: Simple ALU Design

Figure 1 above is a representation of the 2-bit wide ALU indicating its inputs, outputs and a black box chip containing the logical and arithmetic sub circuit blocks. The inputs are 2-bit parallel buses (A0, A1, B0, B1) and a 3-bit opcode (F0, F1, F2) which selects a specific arithmetic, logical or shift operation to be performed by the ALU on the two inputs A and B; and the output is a 2-bit Y (Y0, Y1).

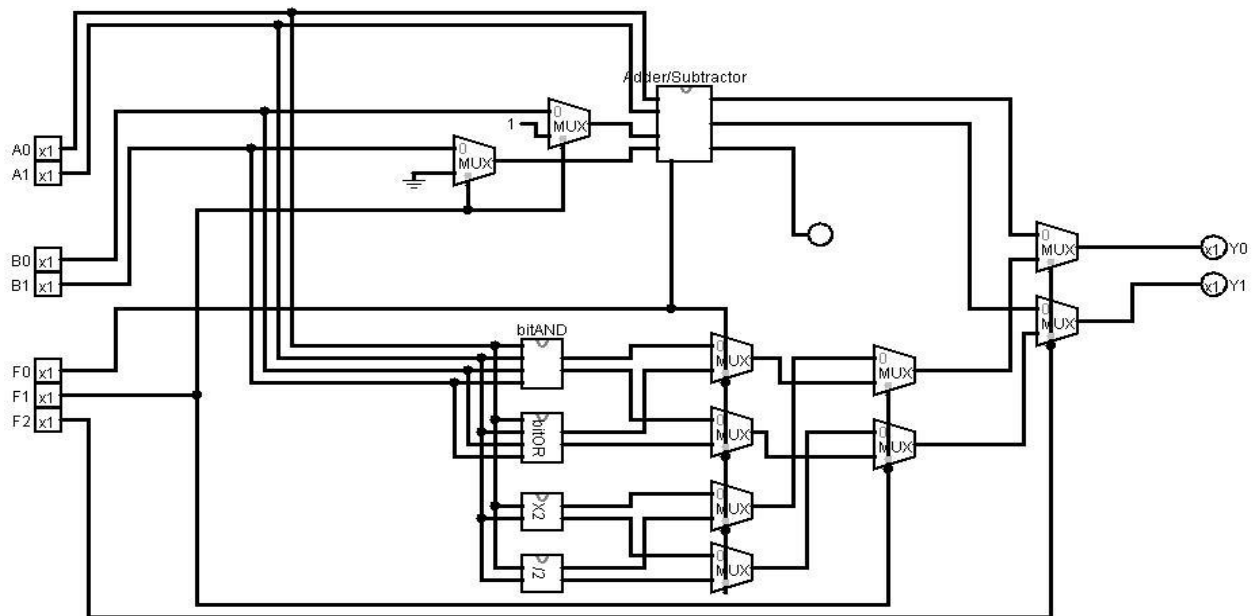


Figure 2: Sub circuits making up the ALU black box chip

Figure 2 above gives a detailed view of all the sub circuits used in making the bigger ALU system with its multiplexers. The sub circuit building blocks used in this report were the Adder/Subtractor block consisting of four sub circuits (namely Addition, Subtraction, Increment and Decrement), Multiply by 2 block (X2), Divide by 2 block (/2), Bitwise AND block (bitAND) and Bitwise OR block (bitOR). These individual sub circuits were interlinked using multiplexers (MUX).

## II. SUB CIRCUIT BUILDING BLOCKS

These are the individual logical, arithmetic and bit shift operations building blocks which form a part of the bigger 2-bit wide ALU system.

### A. ADDER/SUBTRACTOR BLOCK

This block consists of four operations:

#### i) 2-bit Full Addition:

The role of this sub circuit in the bigger system is to give the sum between the two inputs. This gives the sum of two 2-bit inputs including a carry over. *Figure 3* below illustrates that the 2-bit full adder is constructed by adding up two 1-bit full adders with inputs A and B and Cin to give output S and Cout. The Select line is set at 0. From *Figure 4* below, it is seen that B and Sel are connected to an XOR gate and its output is added to its corresponding input A bit using the Adder arithmetic block from Logisim of which gives the final output S. The truth table for this adder sub circuit is shown in *Table 1* below. When the opcode in the ALU is set to '000', this 'Addition' Function is selected and output at Y is the sum of the two inputs A and B.

 


Figure 3: Illustration of a 2-bit Full Adder

#### ii) 2-bit Full Subtraction:

The role of this sub circuit in the bigger system is to give the difference between the two inputs. This gives the difference of two 2-bit inputs including a borrow over. It has two inputs A and B and a borrow bit to give the difference output and borrow. The Select line here is set at 1.

From *Figure 5* below, it is seen that the connections for a 2-bit full subtractor is very similar to that of a 2-bit full Adder except that for the Subtractor, there is inversion of the Select line. Input B and Sel are connected to an XOR gate and its output is added to its corresponding A bit using the Adder arithmetic block from Logisim of which gives the final output S. The truth table for this subtractor sub circuit is shown in *Table 2* below. When the opcode in the ALU is set to '001', this 'Subtraction' Function is selected and the output at Y is the difference of the two inputs A and B.

#### iii) Increment:

The role of this sub circuit in the bigger system is to increase the value of input A by 1. i.e.  $Y = A + 1$ . As seen from *Figure 6*, input B is kept constantly at 1 ( $B_0, B_1 = 1$ ) and the Select line is set at 0 which indicates to add from the previous explanation of 2-bit full Adder. When the opcode in the ALU is set to '010', this 'Increment' function is selected and the output at Y is an increment of A by one.

#### iv) Decrement:

The role of this sub circuit in the bigger system is to decrease the value of input A by 1. i.e.  $Y = A - 1$ . As seen from *Figure 7*, input B is kept constantly at 1 ( $B_0, B_1 = 1$ ) and the Select line is set at 1 which indicates to subtract from the previous explanation of 2-bit full Subtractor. When the opcode in the ALU is set to '011', this 'decrement' function is selected and the output at Y is a decrement of A by one.

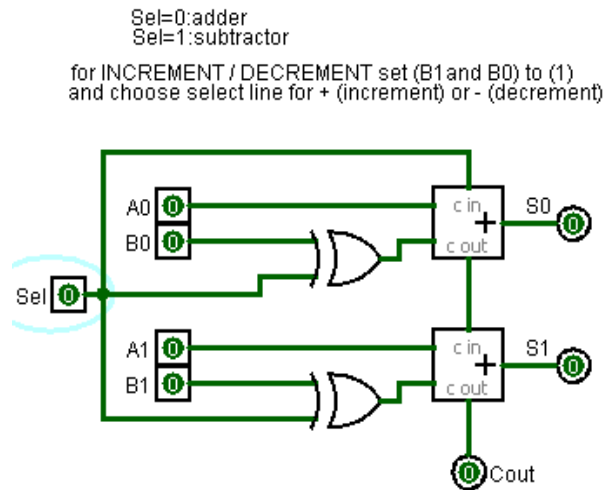


Figure 4: Sub-circuit for 2-bit full Adder block

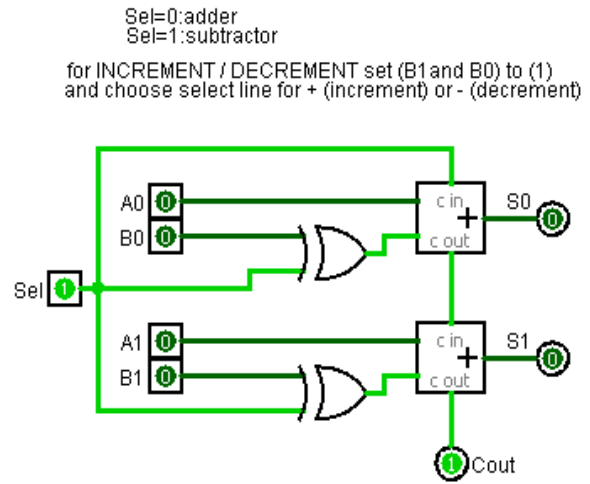


Figure 5: Sub-circuit for 2-bit full Subtractor block

 


Figure 6: Sub circuit for Increment block

 


Figure 7: Sub circuit for Decrement block

Sel	B1	A1	B0	A0	S0	S1	Cout
0	0	0	0	0	0	0	0
0	0	0	0	1	1	0	0
0	0	0	1	0	1	0	0
0	0	0	1	1	0	1	0
0	0	1	0	0	0	1	0
0	0	1	0	1	1	1	0
0	0	1	1	0	1	1	0
0	0	1	1	1	0	0	1
0	1	0	0	0	0	1	0
0	1	0	0	1	1	1	0
0	1	0	1	0	1	1	0
0	1	0	1	1	0	0	1
0	1	1	0	0	0	0	1
0	1	1	0	1	1	0	1
0	1	1	1	0	1	0	1
0	1	1	1	1	0	1	1

Table 1: Truth table for 2-bit Full adder


Sel	B1	A1	B0	A0	S0	S1	Cout
1	0	0	0	0	0	0	1
1	0	0	0	1	1	0	1
1	0	0	1	0	1	1	0
1	0	0	1	1	0	0	1
1	0	1	0	0	0	1	1
1	0	1	0	1	1	1	1
1	0	1	1	0	1	0	1
1	0	1	1	1	0	1	1
1	1	0	0	0	0	1	0
1	1	0	0	1	1	1	0
1	1	0	1	0	1	0	0
1	1	0	1	1	0	1	0
1	1	1	0	0	0	0	1
1	1	1	0	1	1	0	1
1	1	1	1	0	1	1	0
1	1	1	1	1	0	0	1

Table 2: Truth table for 2-bit Full subtractor

### B. MULTIPLY BY 2 BLOCK

The role of this sub circuit in the bigger system is to multiply the value of input A by 2 i.e.  $Y = A * 2$ . In order to achieve this, a 2-bit logical left shifter is used. A logical left shift operation shifts the binary bits of input A to the left and replaces the empty bits by zeros.

As seen from *Figure 8* below, this operation can be constructed using two 1-bit multiplexers and forcing the shift to be 1. The shift has to be 1 in order to achieve a multiplication by 2 because when the shift is 0, the output bit remains same as the corresponding input bit. When Shift =1,  $Y_0 = 0$  and  $Y_1 = A_0$ . When the opcode in the ALU is set to '100', this 'Multiply by 2' function is selected. The truth table for this operation is seen in *Table 3* below.

 

*Figure 8: Sub-circuit for multiply by 2 block*


A1	A0	Y1	Y0
0	0	0	0
0	1	1	0
1	0	0	0
1	1	1	0

*Table 3: Truth table for multiply by 2 block*

### C. DIVIDE BY 2 BLOCK

The role of this sub circuit in the bigger system is to divide the value of input A by 2 i.e.  $Y = A / 2$ . In order to achieve this, a 2-bit logical right shifter is used. A logical right shift operation shifts the binary bits of input A to the right and replaces empty bits by zeros.

As seen from *Figure 9* below, this operation can be constructed using two 1-bit multiplexers and forcing the shift to be 1. The shift has to be 1 in order to achieve a division by 2 because when the shift is 0, the output bit remains same as the corresponding input bit. When Shift =1,  $Y_0 = A_1$  and  $Y_1 = 0$ . When the opcode in the ALU is set to '101', this 'Division by 2' function is selected. The truth table for this operation is seen in *Table 4* below.

 

*Figure 9: Sub-circuit for divide by 2 block*

A1	A0	Y0	Y1
0	0	0	0
0	1	0	0
1	0	1	0
1	1	1	0

*Table 4: Truth table for divide by 2 block*

#### D. BITWISE AND BLOCK

The role of this sub circuit in the bigger system is to compare each bit of input A to the corresponding bit of input B, and iff both bits are 1, only then the corresponding output Y bit is set to 1 otherwise it is set to 0. As seen from *Figure 10* below, this bitwise AND function is obtained by connecting each corresponding input bits of A and B with an AND gate. When the opcode in the ALU is set to '110', this 'bitwise AND' function is selected. The truth table for this operation is seen in *Table 5* below.

 


Figure 10: Sub-circuit for bitwise AND block

B1	A1	B0	A0	Y0	Y1
0	0	0	0	0	0
0	0	0	1	0	0
0	0	1	0	0	0
0	0	1	1	1	0
0	1	0	0	0	0
0	1	0	1	0	0
0	1	1	0	0	0
0	1	1	1	1	0
1	0	0	0	0	0
1	0	0	1	0	0
1	0	1	0	0	0
1	0	1	1	1	0
1	1	0	0	0	1
1	1	0	1	0	1
1	1	1	0	0	1
1	1	1	1	1	1

Table 5: Truth table for bitwise AND block

#### E. BITWISE OR BLOCK

The role of this sub circuit in the bigger system is to compare each bit of input A to the corresponding bit of input B, and if any one or both bits are 1, then the corresponding output Y bit is set to 1. As seen from *Figure 11* below, this bitwise OR function is obtained by connecting each corresponding input bits of A and B with an OR gate. When the opcode in the ALU is set to '111', this 'bitwise OR' function is selected. The truth table for this operation is seen in *Table 6* below.

 


Figure 11: Sub-circuit for bitwise OR block

B1	A1	B0	A0	Y0	Y1
0	0	0	0	0	0
0	0	0	1	1	0
0	0	1	0	1	0
0	0	1	1	1	0
0	1	0	0	0	1
0	1	0	1	1	1
0	1	1	0	1	1
0	1	1	1	1	1
1	0	0	0	0	1
1	0	0	1	1	1
1	0	1	0	1	1
1	0	1	1	1	1
1	1	0	0	0	1
1	1	0	1	1	1
1	1	1	0	1	1
1	1	1	1	1	1

Table 6: Truth table for bitwise OR block