

EEE4117F: ONLINE QUIZ 3

ELECTRICAL MACHINES AND POWER ELECTRONICS



Prepared By:


Ronak Mehta - MHTRON001

Faculty of Engineering and the Built Environment

12th June 2020

PART A – ELECTRICAL MACHINES

Question 1:

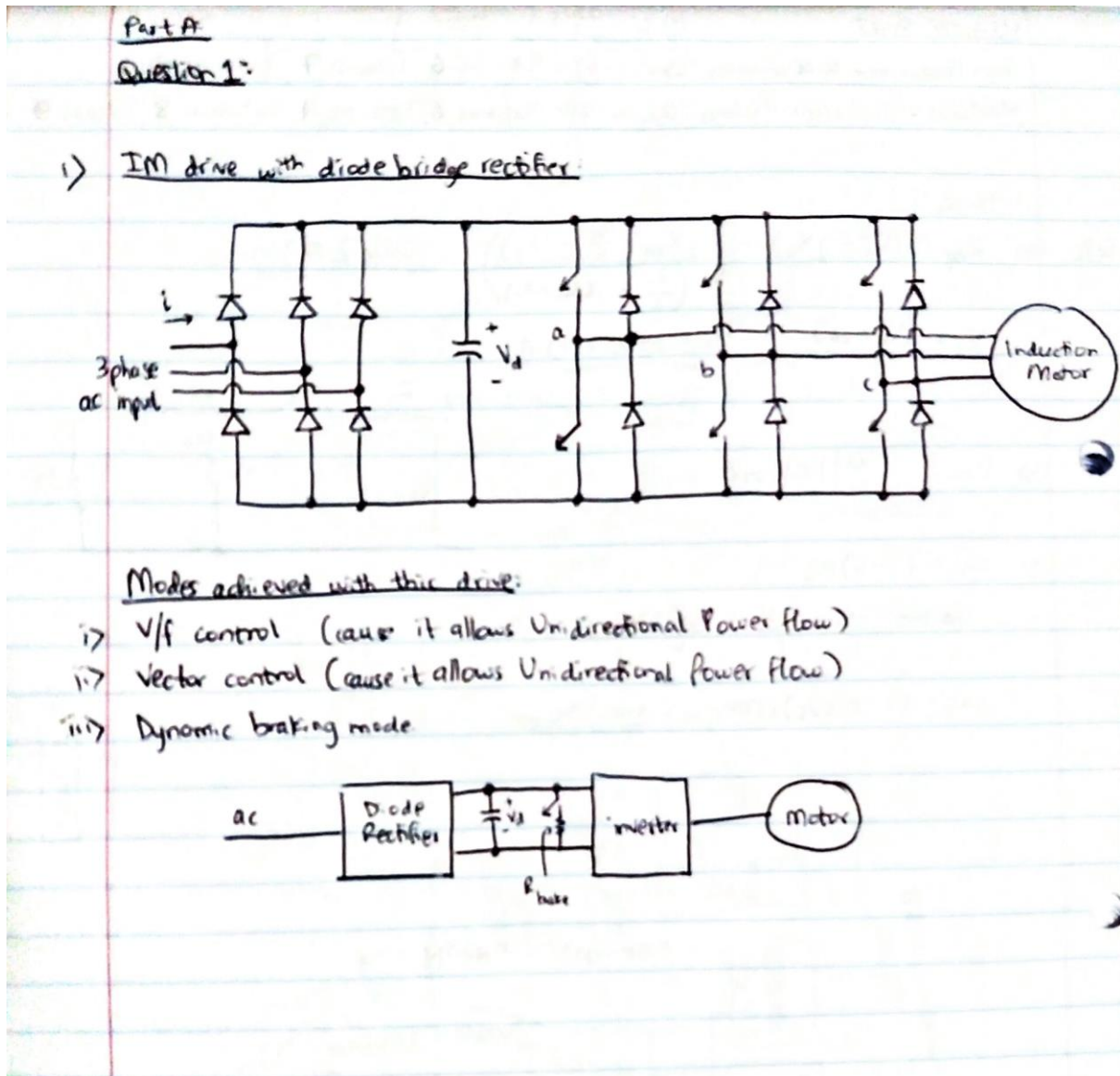

Question 2:

Question 2: Part A

(2.1) @ rated frequency (i.e. 50 Hz)

$$N_s = \frac{120f}{P} = \frac{120(50)}{4} = \underline{1500 \text{ rpm}}$$

$$\text{Slip Speed, } N_{sl} = N_s - N_r = 1500 - 1370 \text{ rpm} = \underline{130 \text{ rpm}}$$

also: @ constant flux:

$$T_{em} = k \omega_{sl} = k N_{sl}$$

@ 80% of full Load Torque:

if Load Torque = 80%, then $N_{sl} = 80\%$ (directly proportional)

$$\therefore N_{sl} \text{ @ } 80\% \text{ of full Load Torque} = 0.8 * 130 \text{ rpm}$$

$$N_{sl_{\text{new}}} = \underline{104 \text{ rpm}}$$

 ~~$N_s = 1500$~~ @ 30 Hz:

$$N_{s_1} = \frac{120(30)}{4} = \underline{900 \text{ rpm}}$$

$$N_{r_1} = N_{s_1} - N_{sl_{\text{new}}}$$

$$= 900 \text{ rpm} - 104 \text{ rpm} = 796 \text{ rpm}$$

$$\therefore \boxed{N_{r_1} = 796 \text{ rpm}}$$

(2.2) @ full-load torque: $N_{sl} = 130 \text{ rpm}$

$$N_s = N_r + N_{sl}$$

$$= 1000 \text{ rpm} + 130 \text{ rpm}$$

$$\therefore \underline{N_s = 1130 \text{ rpm}}$$

$$N_s = \frac{120f}{P} \Rightarrow f = \frac{N_s * P}{120} = \frac{(1130)(4)}{120} = \underline{37.67 \text{ Hz}}$$

$$\therefore \boxed{f = 37.67 \text{ Hz}}$$

(2.3) $f = 40\text{Hz}$, $N_r = 1100\text{rpm}$

$$N_s = \frac{120(40)}{4} = 1200\text{rpm}$$

$$N_{sL} = N_s - N_r = 1200 - 1100 = \underline{100\text{rpm}}$$

@ Full Load; $N_{sL} = 130\text{rpm}$

@ ? Load; $N_{sL} = 100\text{rpm}$

$$100\% T_{em} = 130\text{rpm}$$

$$? T_{em} = 100\text{rpm}$$

$$= \frac{100}{130} \times (100\% T_{em})$$

$$= \underline{76.92\% T_{em}}$$

$\therefore 76.92\%$ of Full-Load Torque is delivered.

(2.4) In regenerative braking mode; N_r exceeds N_s

$$N_s = \frac{120(30)}{4} = 900\text{rpm}$$

from q.1: $N_{sL, \text{new}} = 104\text{rpm}$ (@ 80% of full-load torque)

$$N_r = N_s + N_{sL, \text{new}}$$

$$= 900 + 104$$

$$= \underline{1004\text{rpm}}$$

$$\boxed{N_r = 1004\text{rpm}}$$

PART B – POWER ELECTRONICS

Question 1:

Part B:Question 1:Data:

$$V_o = -12V$$

$$0.46 \leq D \leq 0.545$$

$$R = 15\Omega$$

$$f = 50kHz$$

$$\frac{\Delta V_o}{V_o} < 0.01$$

$$(1.1) \quad D = \frac{|V_o|}{V_d + |V_o|} \Rightarrow V_d = \frac{|V_o| - DV_o}{D}$$

$$V_{d_{max}} = \frac{|V_o| - D_{min}|V_o|}{D_{min}} = \frac{12 - 0.46(12)}{0.46} = \underline{\underline{14.09V}}$$

$$V_{d_{min}} = \frac{12 - 0.545(12)}{0.545} = \underline{\underline{10.02V}}$$

$$\boxed{10.02V \leq V_d \leq 14.09V}$$

Part B: Question 1:

(1-2) $R_L \neq \frac{V_o^2}{P_o}$

$$R_L = \frac{V_o^2}{P_o} = \frac{(-12)^2}{15} = \underline{\underline{9.6 \Omega}}$$

$$L_{\min} = \frac{(1-D)^2 R}{2f}$$

$$1) L_{\min} = \frac{(1-0.46)^2 9.6}{2(50k)} = 28 \mu H$$

$$2) L_{\min} = \frac{(1-0.545)^2 9.6}{2(50k)} = 19.87 \mu H$$

$$\therefore L_{\min} \text{ selected} = 28 \mu H$$

$$\text{But: } L = 1.25 L_{\min} \\ = 1.25(28 \mu H)$$

$$\underline{\underline{L = 35 \mu H}}$$

\therefore The best inductor is $35 \mu H$

$$(1-3) \quad a) C_{\min} = \frac{D}{R \left(\frac{\Delta V_o}{V_o} \right) f} = \frac{0.46}{9.6(0.01)(50k)} = \underline{\underline{95.83 \mu F}}$$

$$b) C_{\min} = \frac{0.545}{9.6(0.01)(50k)} = \underline{\underline{113.5 \mu F}}$$

\therefore Best Capacitor is $113.5 \mu F$

(1-4) Both provides a "Negative Polarity" regulated output Voltage with respect to the common terminal input.

Question 2:

Part B: Question 2:

$$2.1) D = 1 - \frac{V_d}{V_o}$$

$$D_{\max} = 1 - \frac{2.7}{8} = 0.6625$$

$$D_{\min} = 1 - \frac{4.2}{8} = 0.475$$

$$\therefore 0.475 \leq D \leq 0.6625$$

$$\Delta I_L = 0.45 I_L$$

$$I_L = \frac{V_o I_o}{V_d}$$

$$I_L = \frac{8(1)}{2.7} = \underline{2.963A}$$

$$I_L = \frac{8(1)}{4.2} = \underline{1.905A}$$

$$\Delta I_L = 0.45 I_L :$$

$$0.857A \leq \Delta I_L \leq 1.333A$$

$$L_{\min} = \frac{(V_d)D}{(\Delta I_L)f}$$

~~For a Max Lmin~~ For a Max L_{\min} , V_d must be Max, D must be Max and ΔI_L must be Min

$$L_{\min} = \frac{(V_{d\max})D_{\max}}{(\Delta I_{L\min})f} = \frac{(4.2)(0.6625)}{(0.857)(100k)} = \underline{32.47 \mu H}$$

$$\therefore \boxed{L_{\min} = 32.47 \mu H}$$

Part B: Question 2:

$$(2.2) \quad C = \frac{D}{R \left(\frac{\Delta V_o}{V_o} \right) f} \quad ; \quad R = \frac{V_o}{I_o} = \frac{8V}{1A} = \underline{8\Omega}$$

For ~~opt~~ optimal Capacitance:D must Max. and

$$C = \frac{0.6625}{(8)(0.01)(100k)} = \underline{82.8 \mu F}$$

$$\therefore \boxed{C = 82.8 \mu F}$$

NB: when D is min:

$$C = \frac{0.475}{(8)(0.01)(100k)} = \underline{59.4 \mu F}$$

Which is NOT Ideal